
FIFO

Modules

 

My Modules are the following:

- FIFO_RAM.v: Dual RAM Memory used as FIFO Memory.
- DATA_SYNC.v: Double Flipflop Synchronizer to synchronize the Gray encoded Pointers.
- RD_CONTRL.v: FIFO read pointer and Empty flag calculator.
- WR_CONTRL.v: FIFO write pointer and FULL flag calculator.
- FIFO.v: The Top Module Wrapper.

Problem

First the FIFO Problem:

Reading Frequency = 40 MHz "Reading Period = 25ns"

Writing Frequency = 100 MHz "Writing Period = 10ns"

Writing Data Packet size = 10 Byte

Solution:

Time needed to write One Byte = 10ns

Time needed to write the Packet = 100 ns

number of packets to be read = 100/25 = 4 byte

then min FIFO Depth = 10 - 4 = 6 byte

Testbench

Testbench Idea is to send one packet of size 10 bytes and receive it from another size

